

EE309 - POWER SYSTEMS

Assignment-1

Group- 10

Srihith Bansal - 2021EEB1217

Vishakha Agarwal - 2021EEB1221

Vivek Chadgal - 2021EEB1222


Given Problem Statement:

A three-phase 50 Hz transmission line is 400 km long. The sending-end voltage is 220 kV. The line parameters are $r = 0.125 \Omega/\text{km}$, $x = 0.4 \Omega/\text{km}$ and $y = 2.8 \times 10^{-6} \text{ S}/\text{km}$.

Find the following (and answer phasor form) using MATLAB code:

- The A, B, C, and D constants of the line for no-load.
- sending-end current for no-load.
- receiving-end voltage for no-load.
- repeat (a), (b), and (c), assuming the given line is a short transmission line.
- repeat (a), (b), and (c) assuming the given line is a medium transmission line (nominal Π -representation).

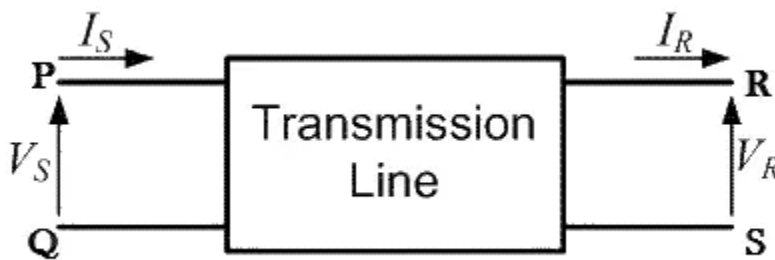A significant section of power system engineering deals with transmitting **electrical power** from one place (e.g. generating station) to another (e.g., **substations** or residential homes) with maximum efficiency.



An input port (PQ) and an output port (RS) comprise a two-port network. It is possible to express the input voltage and input current in terms of the output voltage and output current in any 4 terminal network, such as a linear, passive, or bilateral network. Every port includes two terminals to connect to an external circuit. As a result, it is a circuit with two or four terminals where

Supply End Voltage = V_S

Supply End Current = I_S

Receiving End Voltage = V_R

Receiving end Current = I_R

Thus the relation between the sending and receiving end specifications is given using ABCD parameters by the equations below.

$$\begin{bmatrix} V_S \\ I_S \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_R \\ I_R \end{bmatrix}$$

$$V_S = AV_R + BI_R \dots\dots\dots (1)$$

$$I_S = CV_R + DI_R \dots\dots\dots (2)$$

Therefore, it's critical that power system engineers thoroughly model the transmission of this power. These intricate computations are made simpler by using a two-port model with ABCD parameters.

The receiving end is open-circuited (**No load condition**), meaning the receiving end current $I_R = 0$.

Applying this condition to equation (1) we get,

$$V_S = AV_R + B \cdot 0 \Rightarrow V_S = AV_R + 0$$

$$A = \left. \frac{V_S}{V_R} \right|_{I_R = 0}$$

we get parameter A as the ratio of the sending end voltage to the open circuit receiving end voltage. Since dimension-wise A is a ratio of voltage to voltage, A is a dimensionless parameter.

Applying the same no-load condition i.e. $I_R = 0$, to equation (2)

$$I_S = C V_R + D \cdot 0 \Rightarrow I_S = C V_R + 0$$

$$C = \left. \frac{I_S}{V_R} \right|_{I_R = 0}$$

We get parameter C as the ratio of sending end current to the open circuit receiving end voltage. Since dimension-wise, C is a ratio of current to voltage, and its unit is mho.

Transmission lines are divided into three categories: small transmission lines, medium transmission lines, and long transmission lines, to preserve the precision of the mathematical model. The transmission line's length will affect the formula for these ABCD parameters. This is required because some electrical phenomena only affect long transmission lines, such as corona discharge and the Ferranti effect.

The ABCD parameters of the transmission line can be tabulated as:

Parameter	Specification	Unit
$A = V_S / V_R$	Voltage ratio	Unit less
$B = V_S / I_R$	Short circuit resistance	Ω
$C = I_S / V_R$	Open circuit conductance	mho
$D = I_S / I_R$	Current ratio	Unit less

Code part:

```

1      0 = input('Type (0) for given Parameters/ Type (1) for giving new input parameters: ');
2      %Here we are checking whether the input is user defined or the one given in
3      %the ques
4      if 0==0
5          % Given parameters
6          f = 50; % Frequency (Hz)
7          L = 400; % Line length (km)
8          V_s = 220e3; % Sending-end voltage (V)
9          r = 0.125; % Resistance ( $\Omega$ /km)
10         x = 0.4; % Reactance ( $\Omega$ /km)
11         y = 2.8e-6; % Shunt admittance ( $\text{S}$ /km)
12     else
13         % Taking input from the user
14         f = input('Enter frequency (Hz): ');
15         L = input('Enter line length (km): ');
16         V_s = input('Enter sending-end voltage (V): ');
17         r = input('Enter resistance ( $\Omega$ /km): ');
18         x = input('Enter reactance ( $\Omega$ /km): ');
19         y = input('Enter shunt admittance ( $\text{S}$ /km): ');
20     end
21

```

Here, we first check whether the inputs are user-defined or the one given in the question.

After getting the Resistance (r), Reactance (x), and Admittance (y) values, we can calculate the series impedance and shunt admittance.


Series impedance = $Z = r + jx$

Shunt Admittance = jy

The shunt admittance is defined using the imaginary unit, denoted by 'iota' (i), because admittance is a complex quantity.

```
22     disp(' ')
23     % Line parameters
24     Z = r + 1i*x; % Series impedance
25     Y = 1i*y; % Shunt admittance
26     %Calculate Characteristic impedance
27     Zc = sqrt(Z/Y);
28     % Calculate propagation constant
29     gamma = sqrt(Z*Y);
30     I_r = 0; % At no Load Conditions
31
```

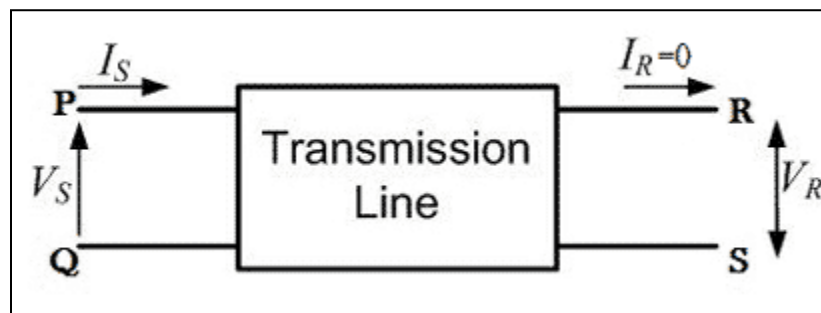Parameters when Receiving end is open-circuited (No load):



Now, we are calculating the Characteristic impedance (Z_c) and propagation constant (γ) in our code.

In no load condition, Receiving end current (I_r) = 0

```

34     disp('Choice of transmission line')
35     disp('0: Long')
36     disp('1: Short')
37     disp('2: Medium -pi Model')
38     v = input('Type of Transmission Line:');

```

Here we are taking input from the user about the type of transmission line.

```

39     if v == 0
40         % No-load constants
41         A = cosh(gamma*L);
42         B = Zc*sinh(gamma*L);
43         C = sinh(gamma*L)/Zc;
44         D = A;
45         disp('Long Transmission Line')
46

```

For the Long Transmission line, ABCD parameters can be calculated by:

$$\begin{aligned}
 A &= \cosh \delta l \\
 B &= Z_C \sinh \delta l \\
 C &= \frac{\sinh \delta l}{Z_C} \\
 D &= \cosh \delta
 \end{aligned}$$

Where delta is gamma.

```

47     elseif v == 1
48         % Short transmission line constants
49         A = 1;
50         B = conj(Z)*L;
51         C = 0;
52         D = A;
53         disp('Short Transmission Line')
54

```

ABCD parameters for the short transmission line.

$$A = 1, B = Z, C = 0, D = 1$$

Here B = Z conjugate

```

55     else
56         % Medium transmission line constants (nominal π-representation)
57         A = 0.5*Z*Y*L*L+1;
58         B = Z*L;
59         C = Y*L*(1+0.25*Z*Y*L*L);
60         D = A;
61         disp('Medium Transmission Line Nominal-π-Model')
62

```

ABCD parameter for Medium Transmission line :

$$A = \left(\frac{Y}{2}Z + 1\right)$$

$$B = Z\left(\frac{Y}{4}Z + 1\right) \Omega$$

$$C = Y \text{ mho}$$

$$D = \left(\frac{Y}{2}Z + 1\right)$$

```

66 M=[A, B; C, D];
67 disp(' ');
68 % Receiving-End Voltage
69 V_r = (V_s - M(1,2)*I_r) / M(1,1);
70
71 %Sending-End Current
72 I_s = (M(2,1)*V_r + M(2,2)*I_r)/sqrt(3);
73
74 disp('ABCD Parameters:');
75 disp(['A = ', num2str(M(1,1))]);
76 disp(['B = ', num2str(M(1,2)), 'ohm']);
77 disp(['C = ', num2str(M(2,1)), 'mho']);
78 disp(['D = ', num2str(M(2,2))]);
79 disp(' ');
80
81 disp('Sending-end Current for No-load:');
82 disp(['I_s = ', num2str(abs(I_s)), ' ∠', num2str(rad2deg(angle(I_s))), ' degrees A']);
83 disp(' ');
84 disp('Receiving-end Voltage for No-load:');
85 disp(['V_r = ', num2str(abs(V_r)/1e3), ' kV ∠', num2str(rad2deg(angle(V_r))), ' degrees']);
86 disp(' ');

```

Now, we are making a matrix for the ABCD parameters. The Receiving end voltage and sending end current can be calculated by equations 1 and 2 mentioned above.

Lastly, we convert the required values into phasor form.

Here it is given a 3 phase transmission line , so we are dividing Is by sqrt (3)

Note:

Here in the code we have taken the units of parameters as :

- Frequency - Hz
- Line length - Km
- Sending end Voltage - KV
- Resistance - Ω /Km
- Reactance - Ω /Km
- Admittance - S/Km

For other units , first change it into the units mentioned above .

```

>> Group_10_Assi_1
Type (0) for given Parameters/ Type (1) for giving new input parameters: 0

Choice of transmission line
0: Long
1: Short
2: Medium -pi Model
Type of Transmission Line:2
Medium Transmission Line Nominal- $\Pi$ -Model

ABCD Parameters:
A = 0.9104+0.028i
B = 50+160iohm
C = -1.568e-05+0.0010698imho
D = 0.9104+0.028i

Sending-end Current for No-load:
I_s = 149.205  $\angle$ 89.0781 degrees A

Receiving-end Voltage for No-load:
V_r = 241.5378 kV  $\angle$ -1.7616 degrees

```

Answers for the medium line transmission with the given input parameters in the question.

```

Enter frequency (Hz): 50
Enter line length (km): 50
Enter sending-end voltage (V): 220e3
Enter resistance ( $\Omega$ /km): 0.125
Enter reactance ( $\Omega$ /km): 0.4
Enter shunt admittance ( $\text{U}$ /km): 2.8e-6

Choice of transmission line
0: Long
1: Short
2: Medium -pi Model
Type of Transmission Line:1
Short Transmission Line

ABCD Parameters:
A = 1
B = 6.25-20iohm
C = 0mho
D = 1

Sending-end Current for No-load:
I_s = 0  $\angle$ 0 degrees A

Receiving-end Voltage for No-load:
fx V_r = 220 kV  $\angle$ 0 degrees

```

Answers for Short Line Transmission line


```

Enter frequency (Hz): 50
Enter line length (km): 500
Enter sending-end voltage (V): 220e3
Enter resistance ( $\Omega/\text{km}$ ): 0.125
Enter reactance ( $\Omega/\text{km}$ ): 0.4
Enter shunt admittance ( $\text{S}/\text{km}$ ): 2.8e-6

```

```
Choice of transmission line
```

```
0: Long
```

```
1: Short
```

```
2: Medium -pi Model
```

```
Type of Transmission Line:0
```

```
Long Transmission Line
```

```
ABCD Parameters:
```

```
A = 0.86293+0.041736i
```

```
B = 56.7842+191.6701iohm
```

```
C = -1.9851e-05+0.0013355imho
```

```
D = 0.86293+0.041736i
```

```
Sending-end Current for No-load:
```

```
Is = 196.3672  $\angle$ 88.0826 degrees A
```

```
Receiving-end Voltage for No-load:
```

```
fx Vr = 254.6488 kV  $\angle$ -2.769 degrees
```

Answers for Long Transmission lines

Conclusion:

The line parameters provided are per-phase values. The analysis conducted through MATLAB provides insight into the behavior of the transmission line under various assumptions. It allows us to understand the performance characteristics such as sending-end current and receiving-end voltage under different transmission line models. By comparing the results obtained for short, medium, and general transmission line models, we can infer the impact of line parameters on transmission line behavior and performance.